



KERALA AGRICULTURAL UNIVERSITY  
B. Tech. (Agrl. Engg.) 2020 Admission  
IV Semester Final Examination – August 2022

Sacs.2213

Applied Electronics and Instrumentation (2+1)

Marks: 50  
Time: 2 hours

**I Fill in the blanks**

(10x1=10)

1. The atomic number of silicon is\_\_\_\_\_.
2. The energy band in which free electrons exists is\_\_\_\_\_.
3. The type of diode used for voltage regulation is\_\_\_\_\_.
4. CMRR of an op-amp should be \_\_\_\_\_.
5. The first point of contact in any measurement system is\_\_\_\_\_.

**State True or False**

6. Zener breakdown happens in forward biasing.
7. Oscillators do not need a power source to work.
8. An ideal Op-Amp has infinite gain.
9. The thermocouple working principle is based on the Seebeck Effect.
10. Load cells used the principle of strain gauges.

**II Write short notes on ANY FIVE of the following**

(5x2=10)

1. Summarize the concept of Semiconductors.
2. Identify the types of rectifiers.
3. Differentiate between clipper and clamper.
4. List the characteristics of an ideal OP-AMP.
5. Write short notes on half adders.
6. What is a transducer?
7. Briefly explain force measurement using load cells.

**III Answer ANY FIVE of the following**

(5x4=20)

1. Explain the V-I characteristics of P-N junction diode.
2. Distinguish the half-wave and the full-wave rectifiers.
3. Summarize the concept of the Wein bridge oscillator.
4. Identify the operation of Op-Amp as integrator and differentiator.
5. Explain the features of the bipolar junction transistor.
6. Classify the pressure measurement transducers.
7. Describe any one transducer for the measurement of displacement.

**IV Write an essay on ANY ONE of the following**

(1x10=10)

1. With a neat block schematic explain the generalised instrumentation system in detail.
2. Distinguish the various biasing methods of the bipolar junction transistor.

\*\*\*\*\*